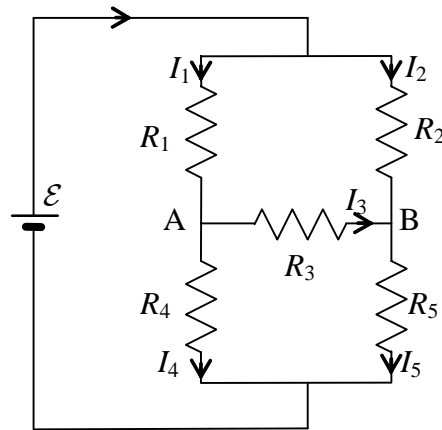


Example of Use of Kirchoff's Rules



What is the effective resistance of the network above? When connected to a source of EMF as shown, what are the potentials at points A & B (with respect to the negative side of the battery)?

Use the following component values: $\mathcal{E} = 3 \text{ V}$, $R_1 = 3 \Omega$, $R_2 = 4 \Omega$, $R_3 = 10 \Omega$, $R_4 = 7 \Omega$, $R_5 = 4 \Omega$.

Applying Kirchoff's junction rule at A: $I_1 - I_3 - I_4 = 0$ (1)

Applying Kirchoff's junction rule at B: $I_2 + I_3 - I_5 = 0$ (2)

Applying Kirchoff's loop rule: clockwise, upper loop:
 $-I_2 R_2 + I_3 R_3 + I_1 R_1 = 0$ (3)

Applying Kirchoff's loop rule: clockwise, lower loop:
 $-I_5 R_5 + I_4 R_4 - I_3 R_3 = 0$ (4)

Applying Kirchoff's loop rule: clockwise, left loop:
 $\mathcal{E} - I_1 R_1 - I_4 R_4 = 0$ (5)

(Note: we have 5 unknowns – the 5 currents – so require 5 independent equations.)

(1) $\Rightarrow I_3 = I_1 - I_4$ (1')

(2) $\Rightarrow I_3 = I_5 - I_2$
 $\Rightarrow I_5 - I_2 = I_1 - I_4$ (2')

(3) $\Rightarrow -I_2 R_2 + (I_1 - I_4) R_3 + I_1 R_1 = 0$ (6)

(4) $\Rightarrow -I_5 R_5 + I_4 R_4 - (I_1 - I_4) R_3 = 0$ (7)

(6) $\times R_5 - (7) \times R_2 \Rightarrow -I_2 R_2 R_5 + (I_1 - I_4) R_3 R_5 + I_1 R_1 R_5 - (-I_5 R_2 R_5 + I_4 R_2 R_4 - (I_1 - I_4) R_2 R_3) = 0$

$\Rightarrow (I_5 - I_2) R_2 R_5 + (I_1 - I_4) R_3 R_5 + I_1 R_1 R_5 - I_4 R_2 R_4 + (I_1 - I_4) R_2 R_3 = 0$

Or, using (2') $(I_1 - I_4)(R_2 R_5 + R_3 R_5 + R_2 R_3) + I_1 R_1 R_5 - I_4 R_2 R_4 = 0$

It is probably easier at this point to substitute in the component values:

$$(4 \times 4 + 10 \times 4 + 4 \times 10)(I_1 - I_4) + 3 \times 4 I_1 - 4 \times 7 I_4 = 0$$

$$108I_1 - 124I_4 = 0 \quad \Rightarrow \quad I_4 = \frac{108}{124}I_1 = \frac{27}{31}I_1$$

$$(5) \Rightarrow \quad \mathcal{E} - I_1R_1 - I_4R_4 = 0 \quad \Rightarrow \quad 3 - 3I_1 - 7 \times \frac{27}{31}I_1 = 0$$

$$\Rightarrow \quad I_1 = 0.330 \text{ A} \quad I_4 = \frac{27}{31}I_1 = 0.287 \text{ A}$$

$$(1) \Rightarrow \quad I_3 = I_1 - I_4 = 0.043 \text{ A}$$

$$(3) \Rightarrow \quad -4I_2 + 10I_3 + 3I_1 = 0 \quad \Rightarrow \quad I_2 = \frac{10I_3 + 3I_1}{4} = 0.355 \text{ A}$$

$$(2) \Rightarrow \quad I_5 = I_2 + I_3 = 0.398 \text{ A}$$

$$I_{\text{Total}} = I_1 + I_2 = 0.685 \text{ A}$$

$$\text{Effective resistance} \quad R_{\text{Eff}} = \frac{\mathcal{E}}{I_{\text{Total}}} = \frac{3}{0.685} = 4.38 \Omega$$

$$V_A = I_4R_4 = 0.287 \times 7 = 2.009 \text{ V}$$

$$V_B = I_5R_5 = 0.398 \times 4 = 1.592 \text{ V}$$